


**1998 System Wiring Diagrams**

**Kia - Sportage**

**ANTI-THEFT**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

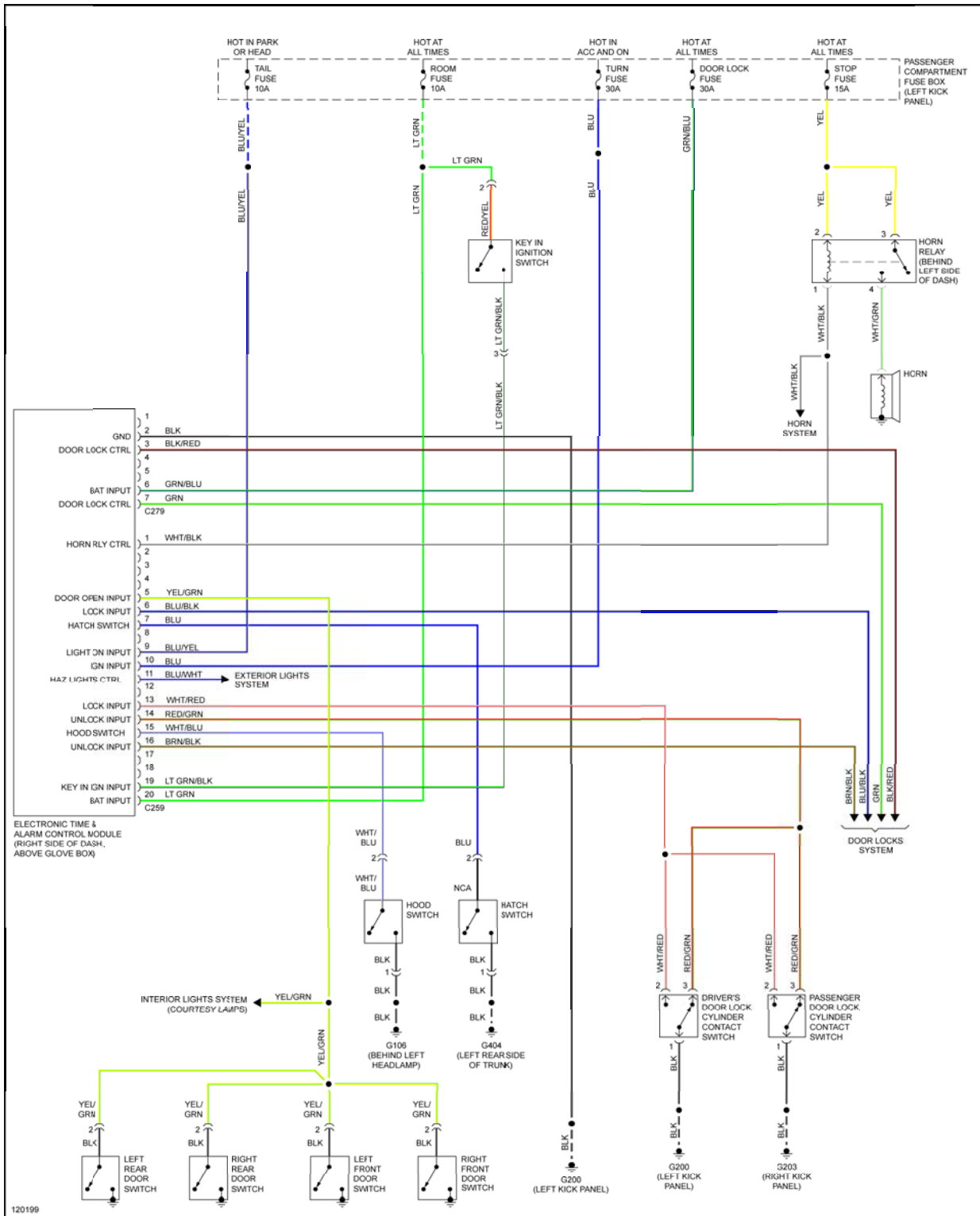


**Fig. 1: Anti-theft Circuit**

**COMPUTER DATA LINES**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

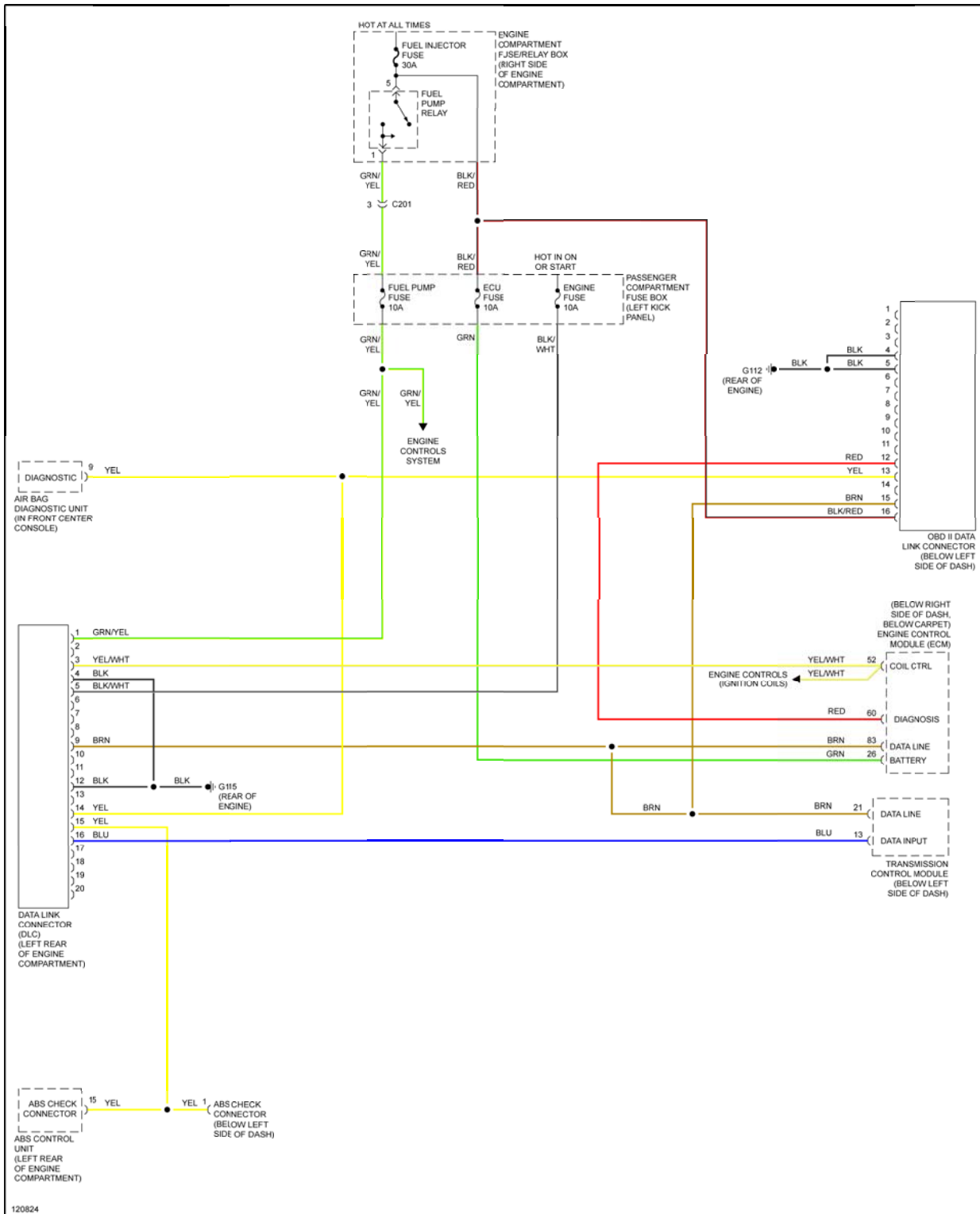

**Fig. 2: Computer Data Lines**

**COOLING FAN**

## SYSTEM WIRING DIAGRAMS



**Fig. 3: Condenser Cooling Fan Circuit**

**CRUISE CONTROL**

## SYSTEM WIRING DIAGRAMS

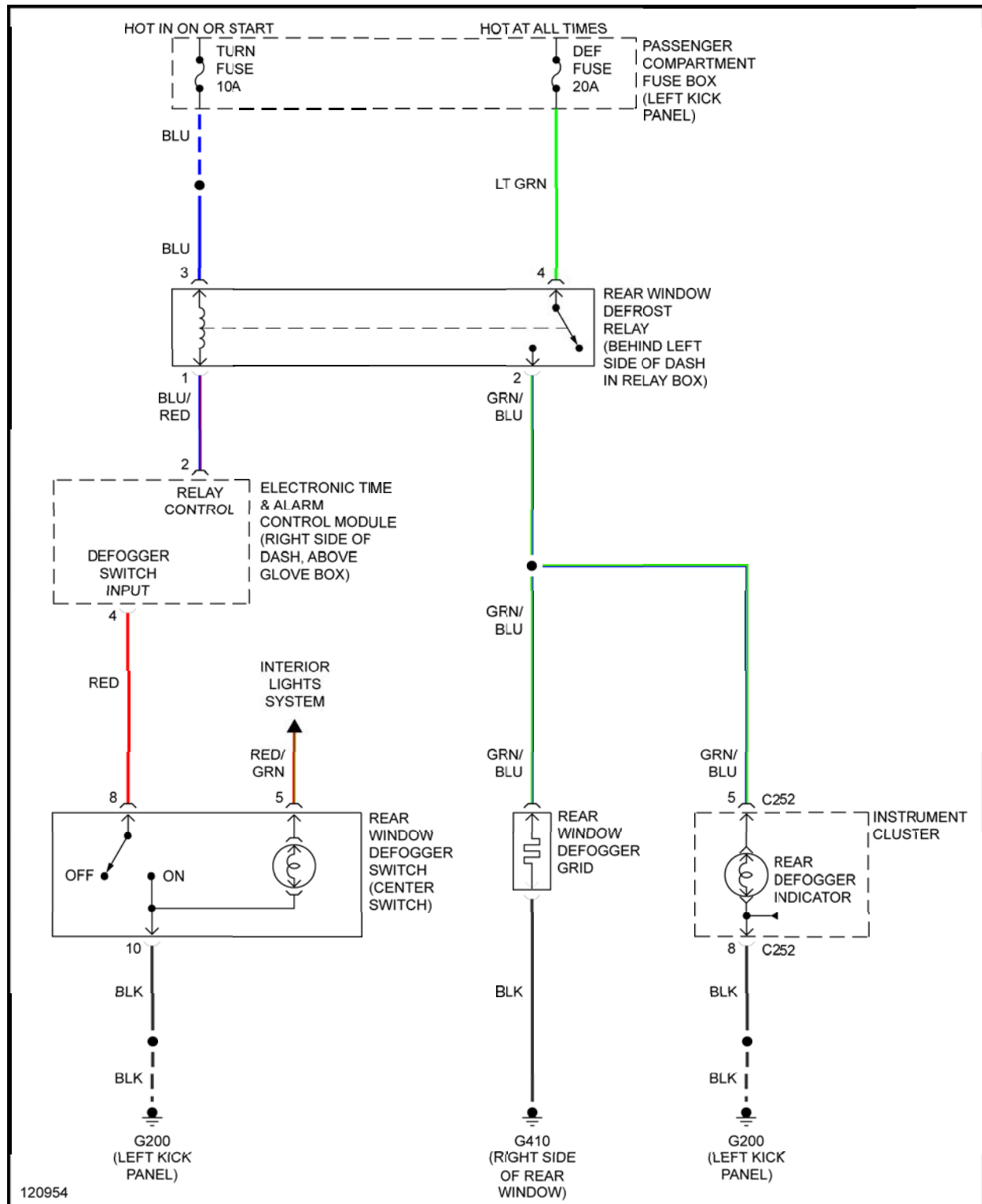


**Fig. 4: Cruise Control Circuit**

**DEFOGGERS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

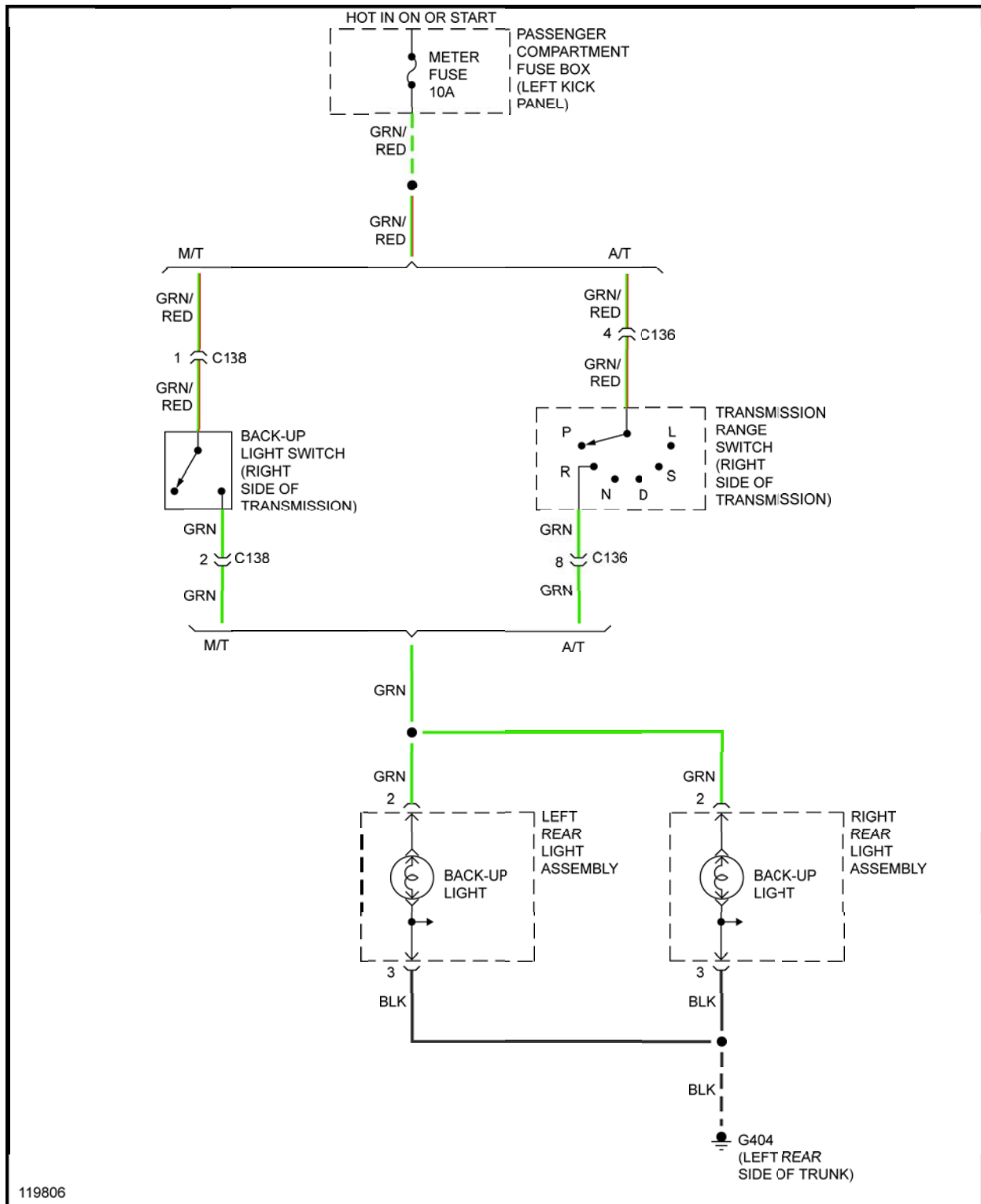


**Fig. 5: Defogger Circuit**

**EXTERIOR LIGHTS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS



**Fig. 6: Back-up Lamps Circuit**

## SYSTEM WIRING DIAGRAMS

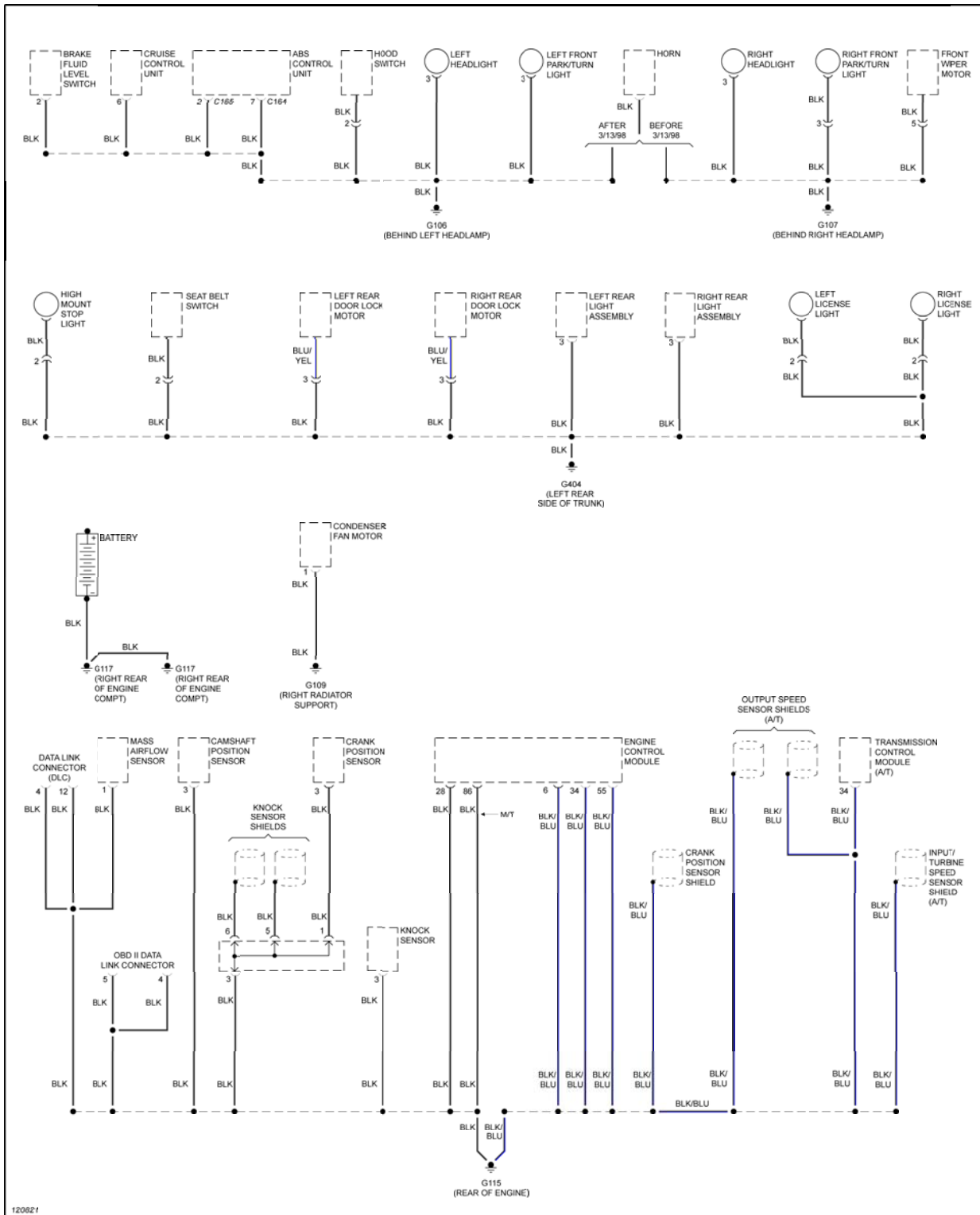


**Fig. 7: Exterior Lamps Circuit**

**GROUND DISTRIBUTION**

# 1998 Kia Sportage


## SYSTEM WIRING DIAGRAMS



**Fig. 8: Ground Distribution Circuit (1 of 2)**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

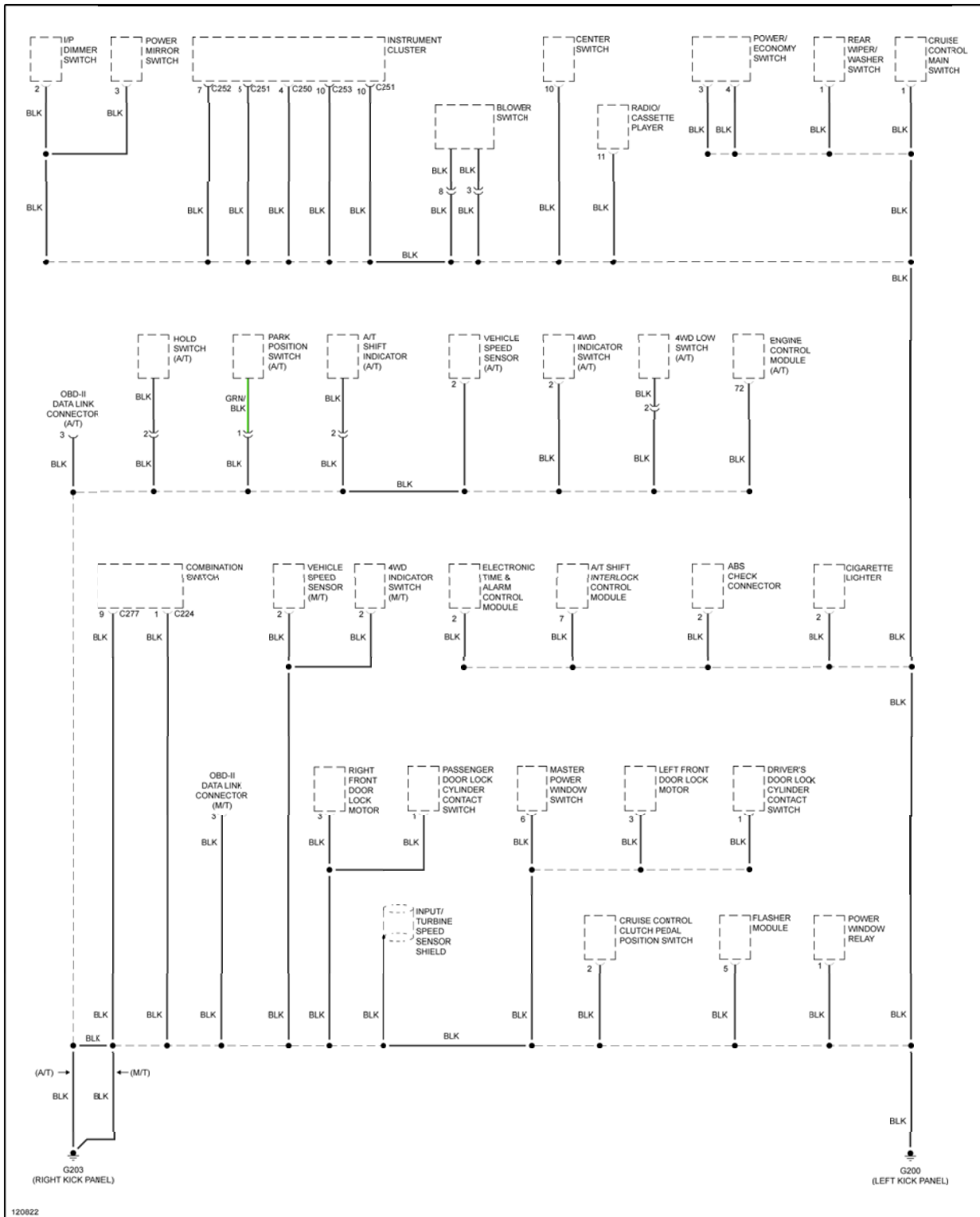


**Fig. 9: Ground Distribution Circuit (2 of 2)**

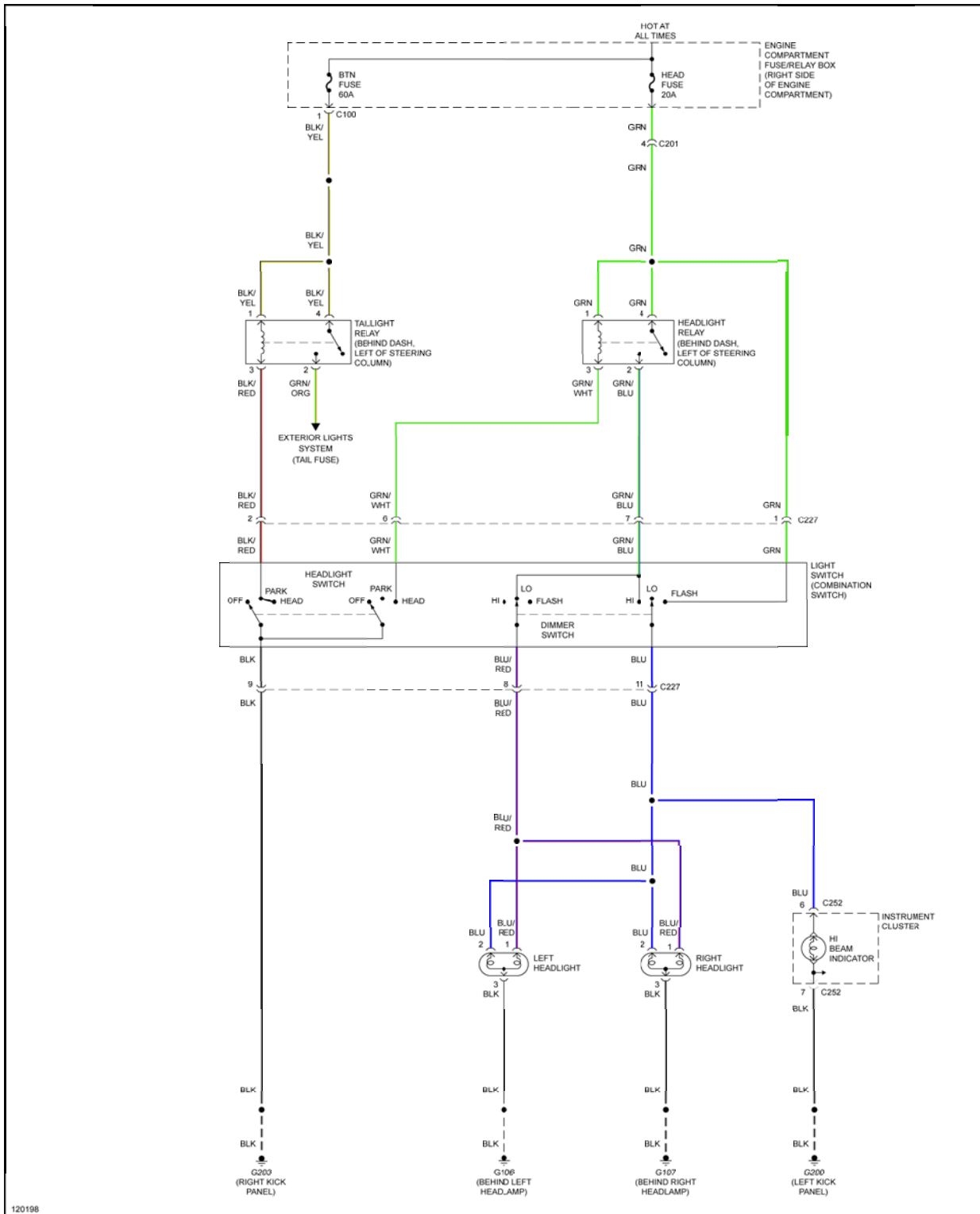**HEADLIGHTS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS




120198

**Fig. 10: Headlight Circuit**

**HORN**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

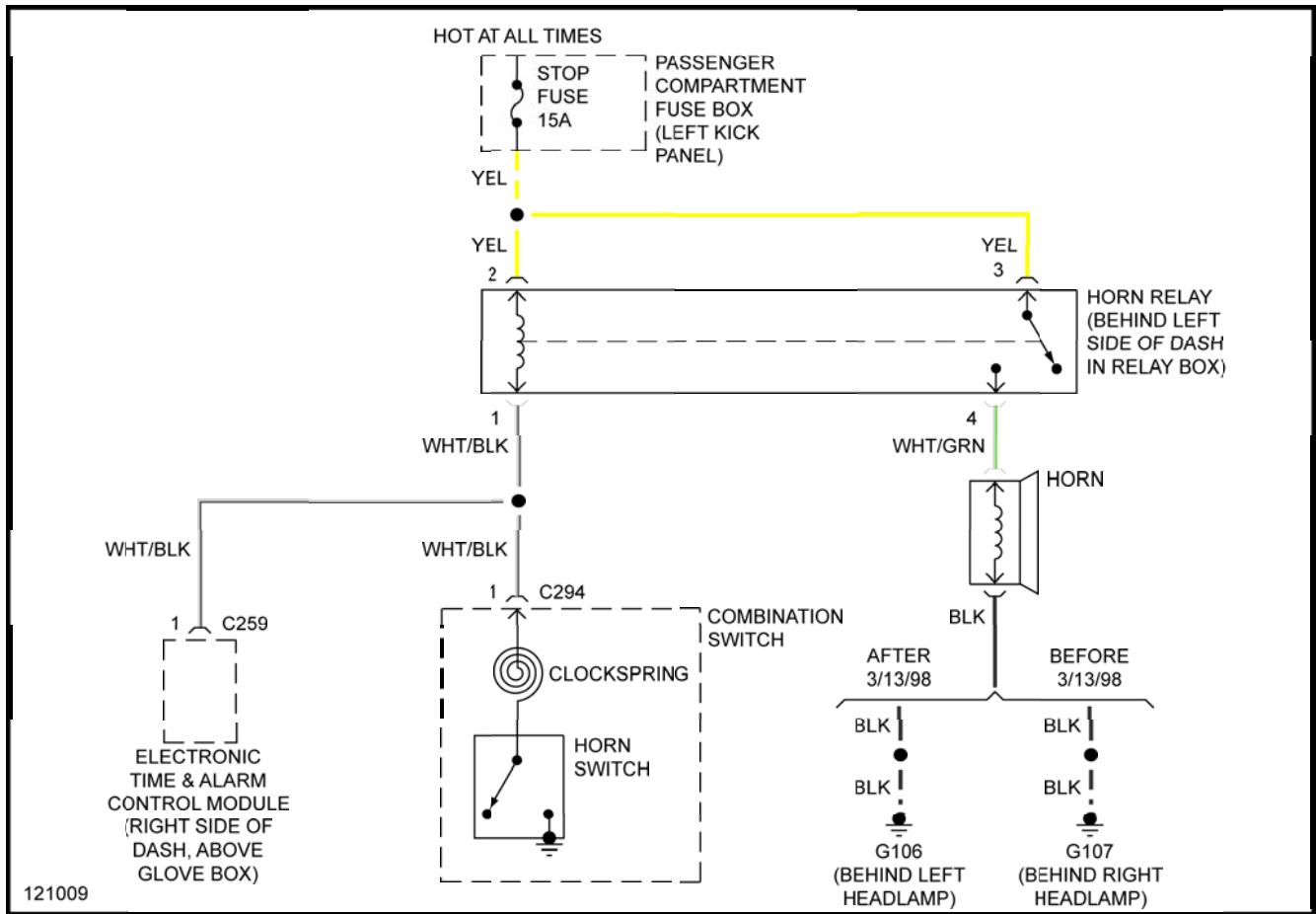


**Fig. 11: Horn Circuit**

**INSTRUMENT CLUSTER**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

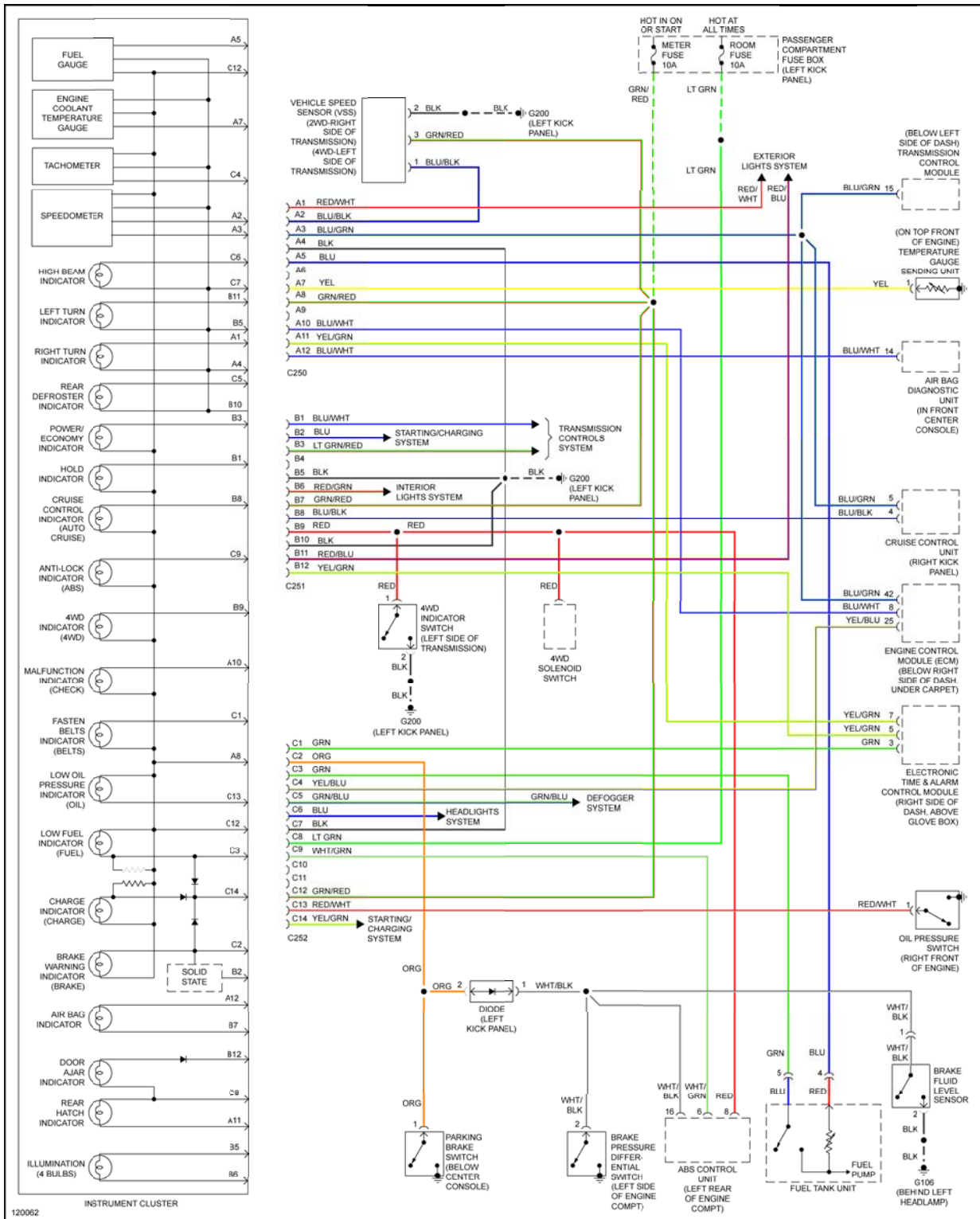


**Fig. 12: Instrument Cluster Circuit**

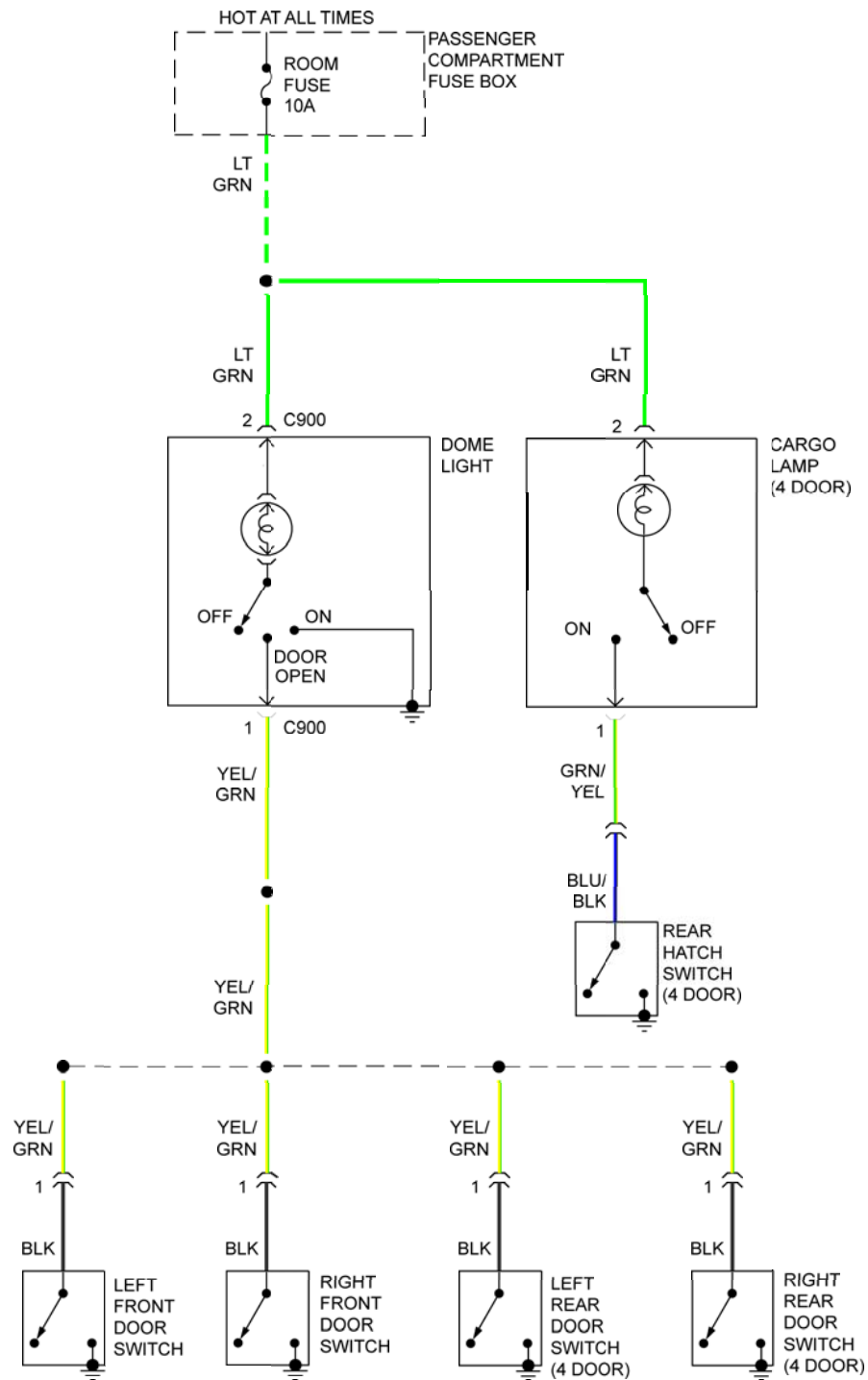**INTERIOR LIGHTS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS



120059

**Fig. 13: Courtesy Lamps Circuit**

## SYSTEM WIRING DIAGRAMS

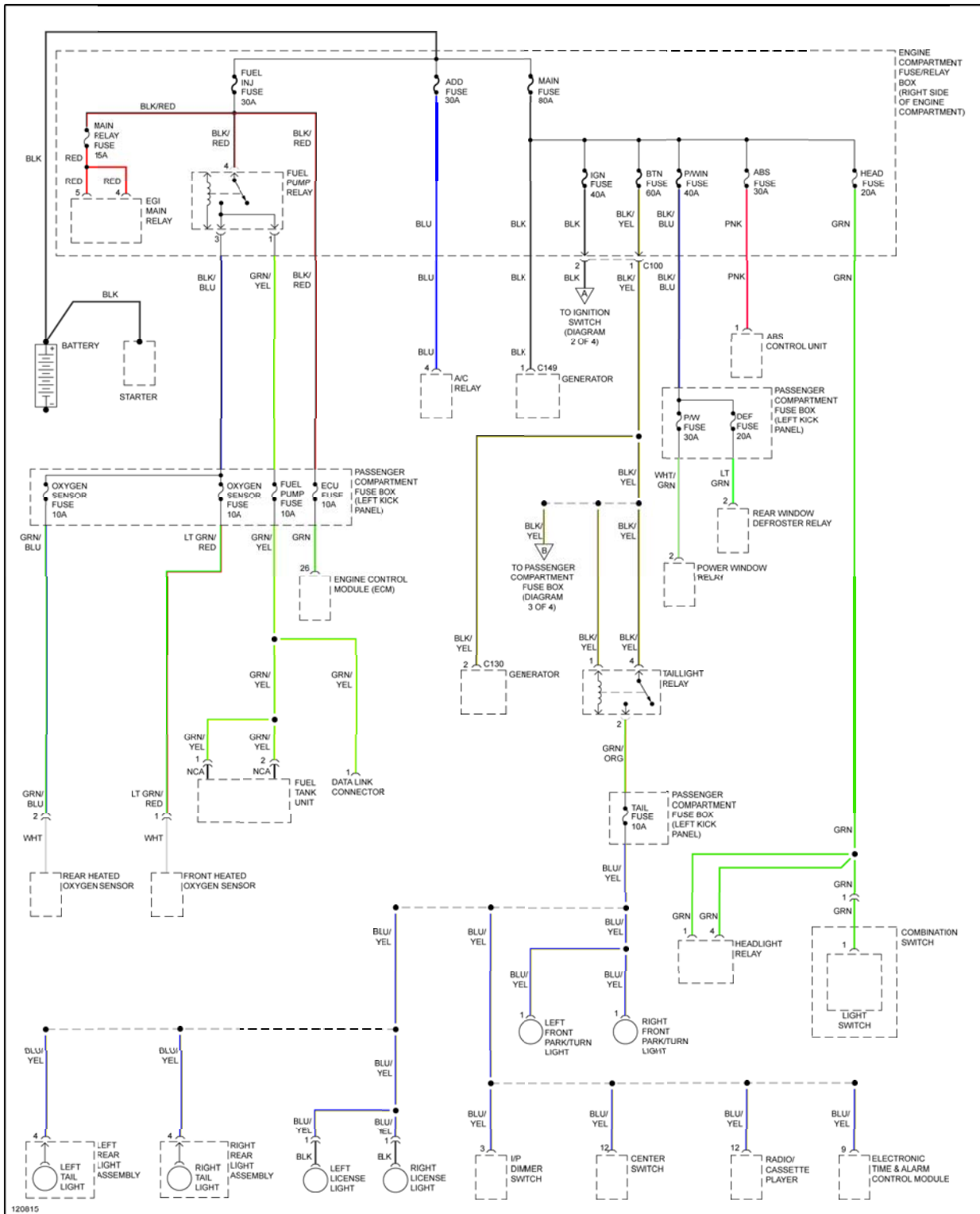


**Fig. 14: Instrument Illumination Circuit**

**POWER DISTRIBUTION**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS



**Fig. 15: Power Distribution Circuit (1 of 4)**


## SYSTEM WIRING DIAGRAMS



**Fig. 16: Power Distribution Circuit (2 of 4)**

# 1998 Kia Sportage


## SYSTEM WIRING DIAGRAMS

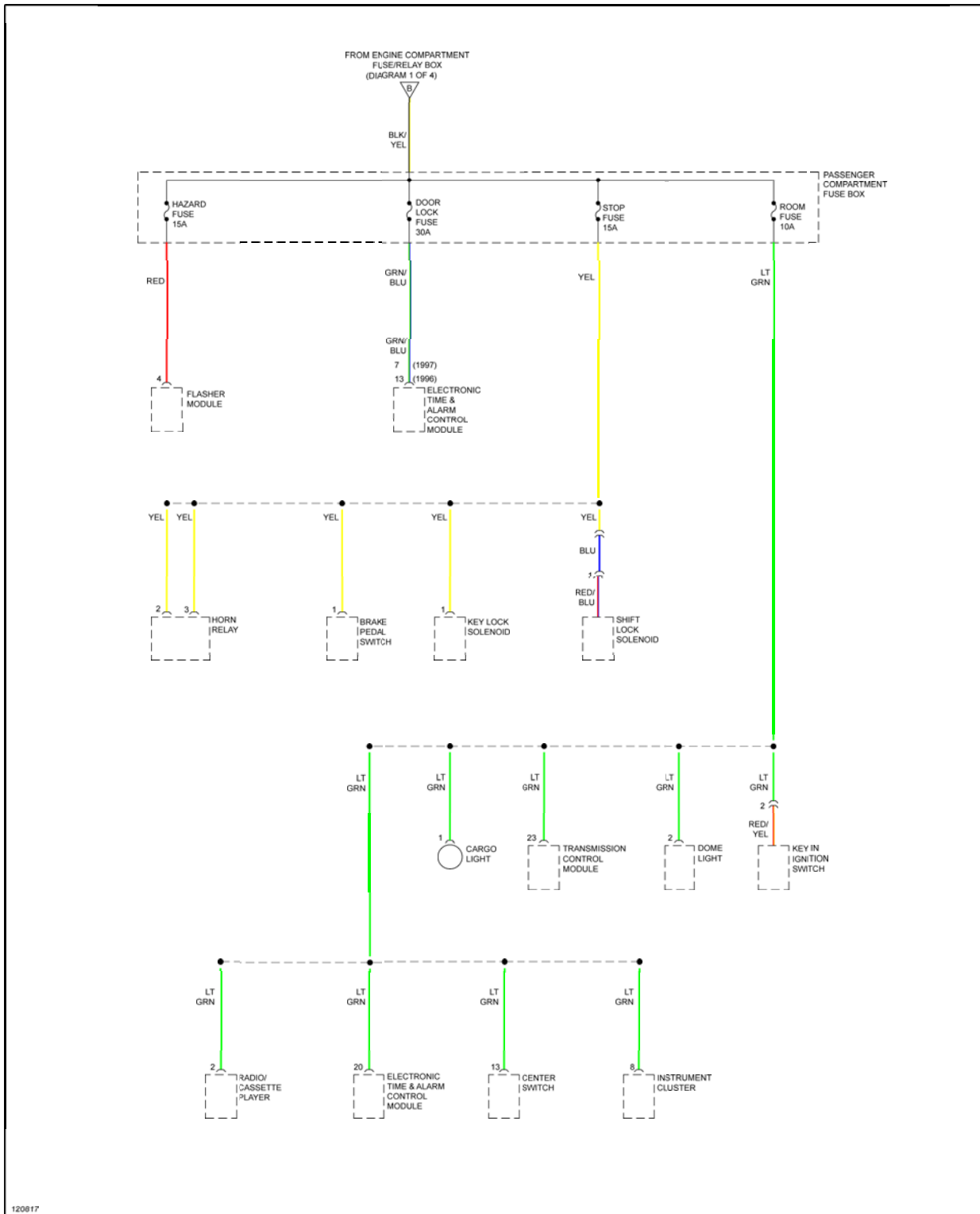

**Fig. 17: Power Distribution Circuit (3 of 4)**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

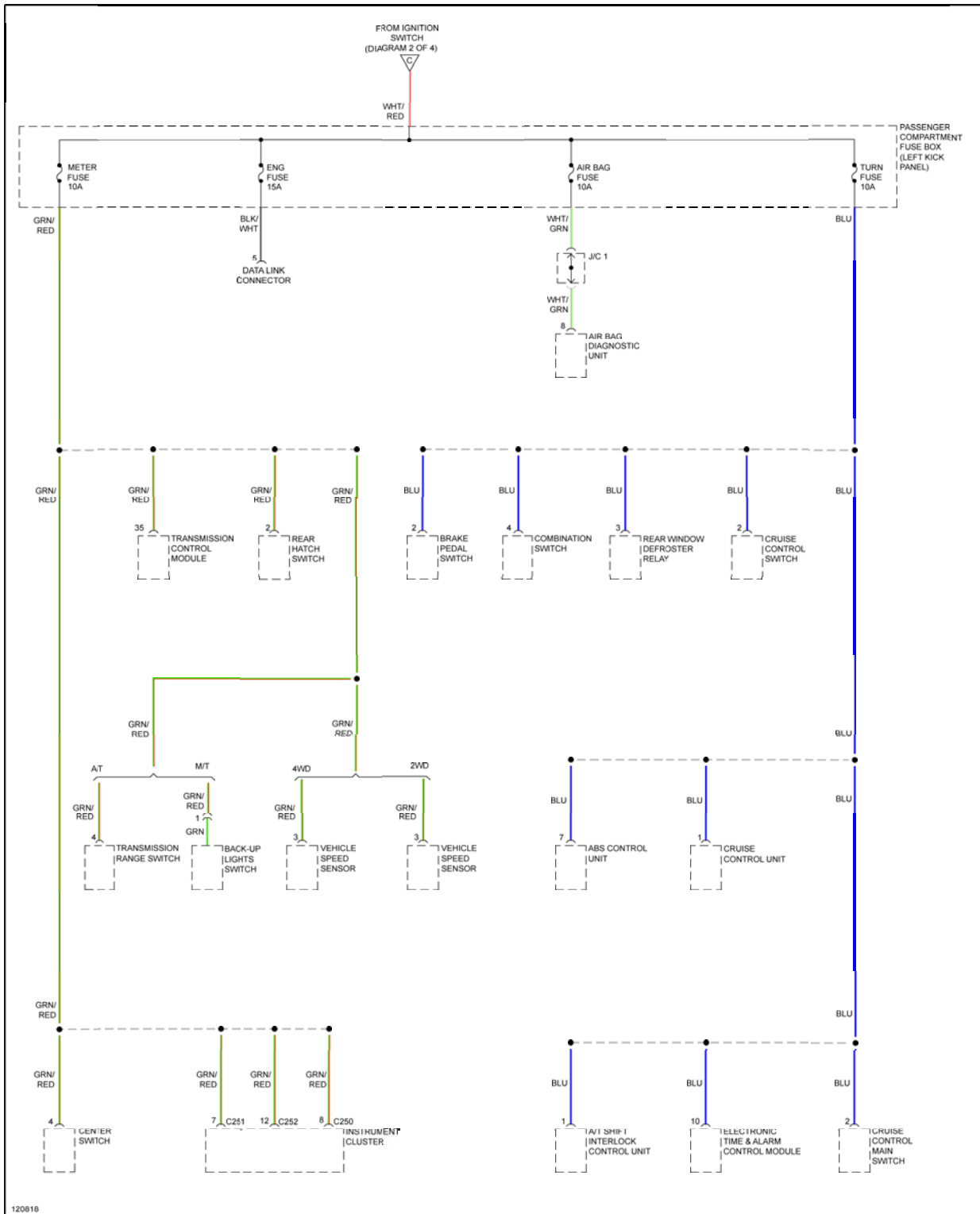

**Fig. 18: Power Distribution Circuit (4 of 4)**

**POWER DOOR LOCKS**


## SYSTEM WIRING DIAGRAMS



**Fig. 19: Power Door Lock Circuit, 2 Door**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

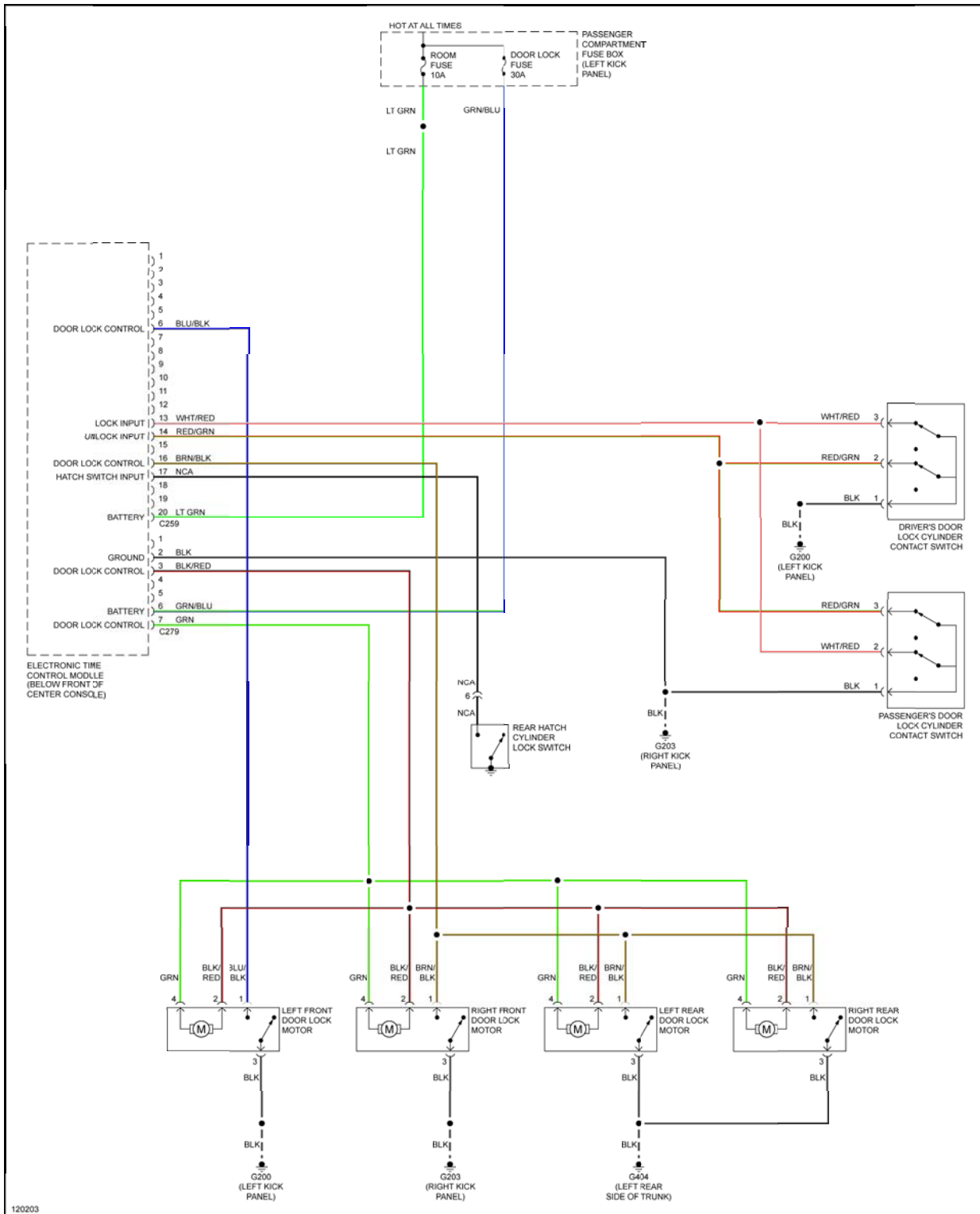


**Fig. 20: Power Door Lock Circuit, 4 Door**

**POWER MIRRORS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

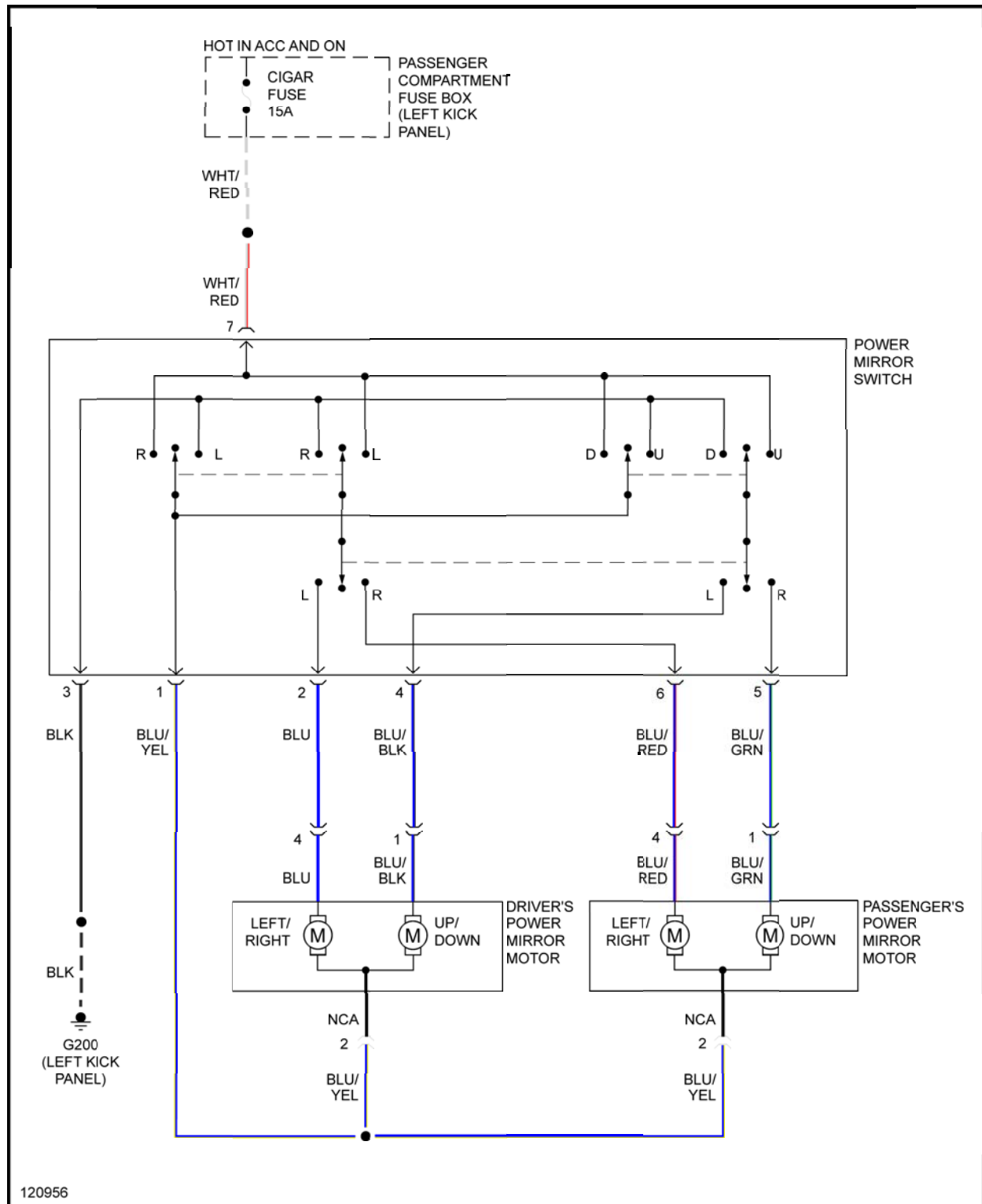


**Fig. 21: Power Mirror Circuit**

**POWER WINDOWS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

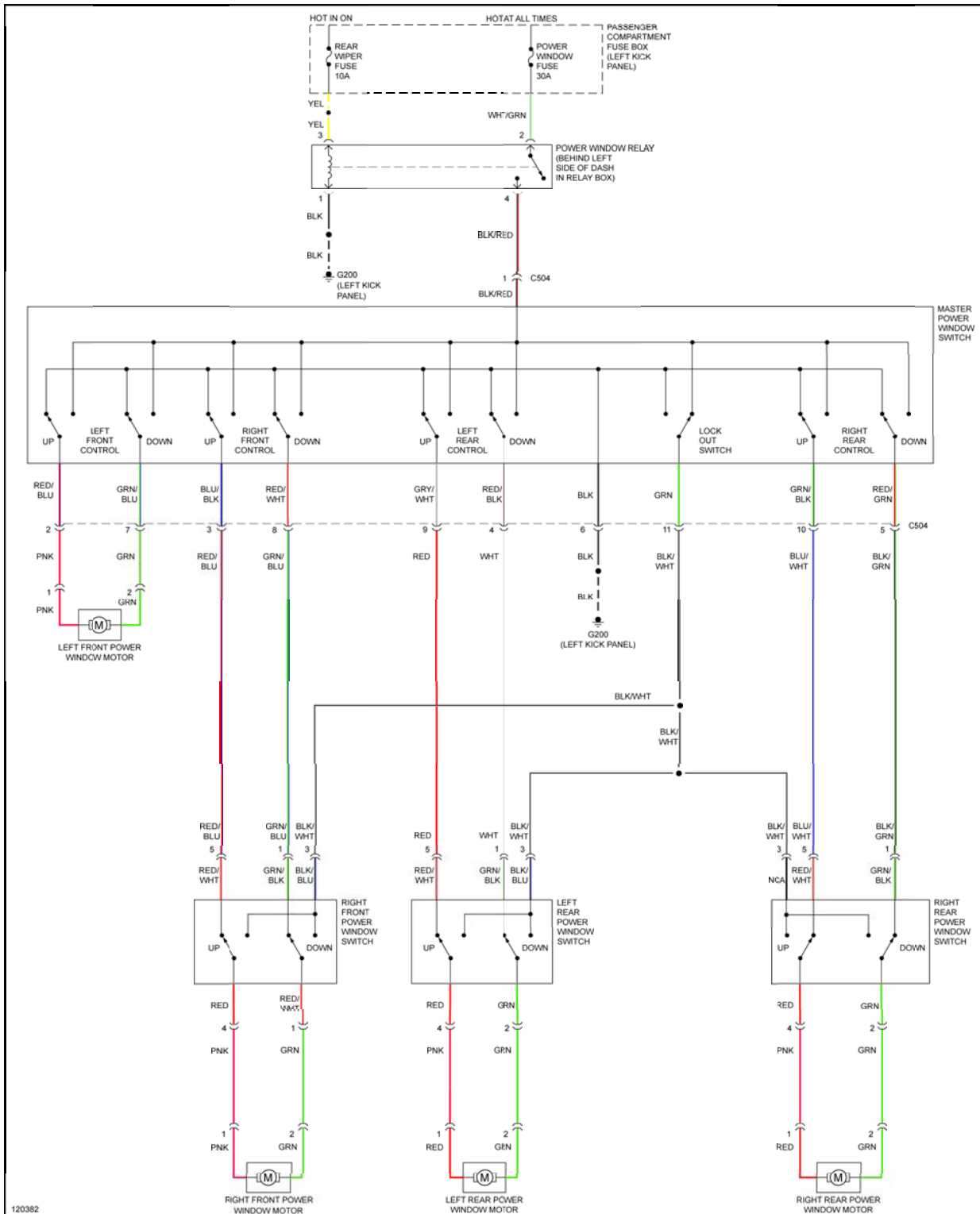


**Fig. 22: Power Window Circuit**

**RADIO**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

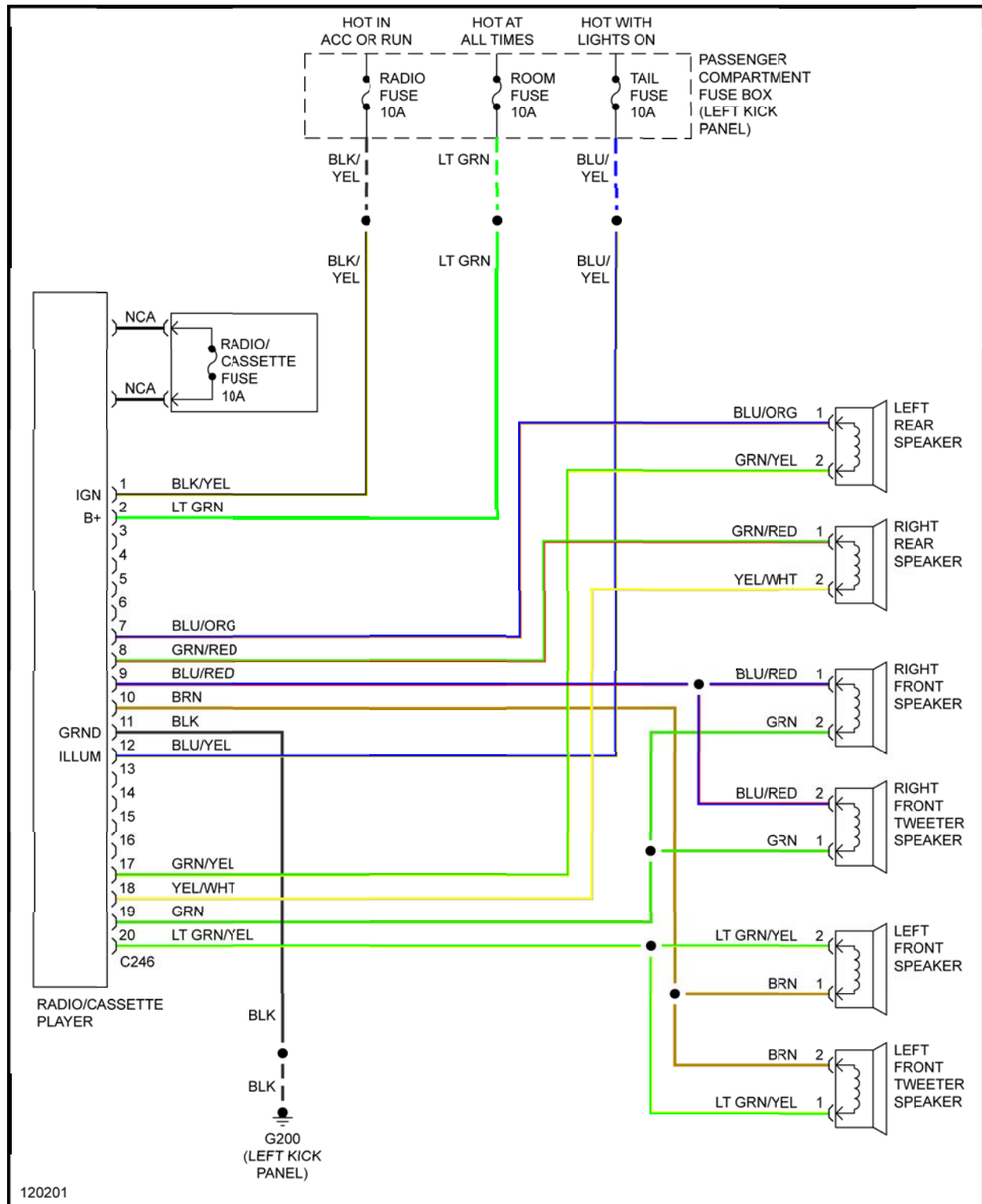


**Fig. 23: Stereo Radio/Tape Player Circuit**

**SHIFT INTERLOCKS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

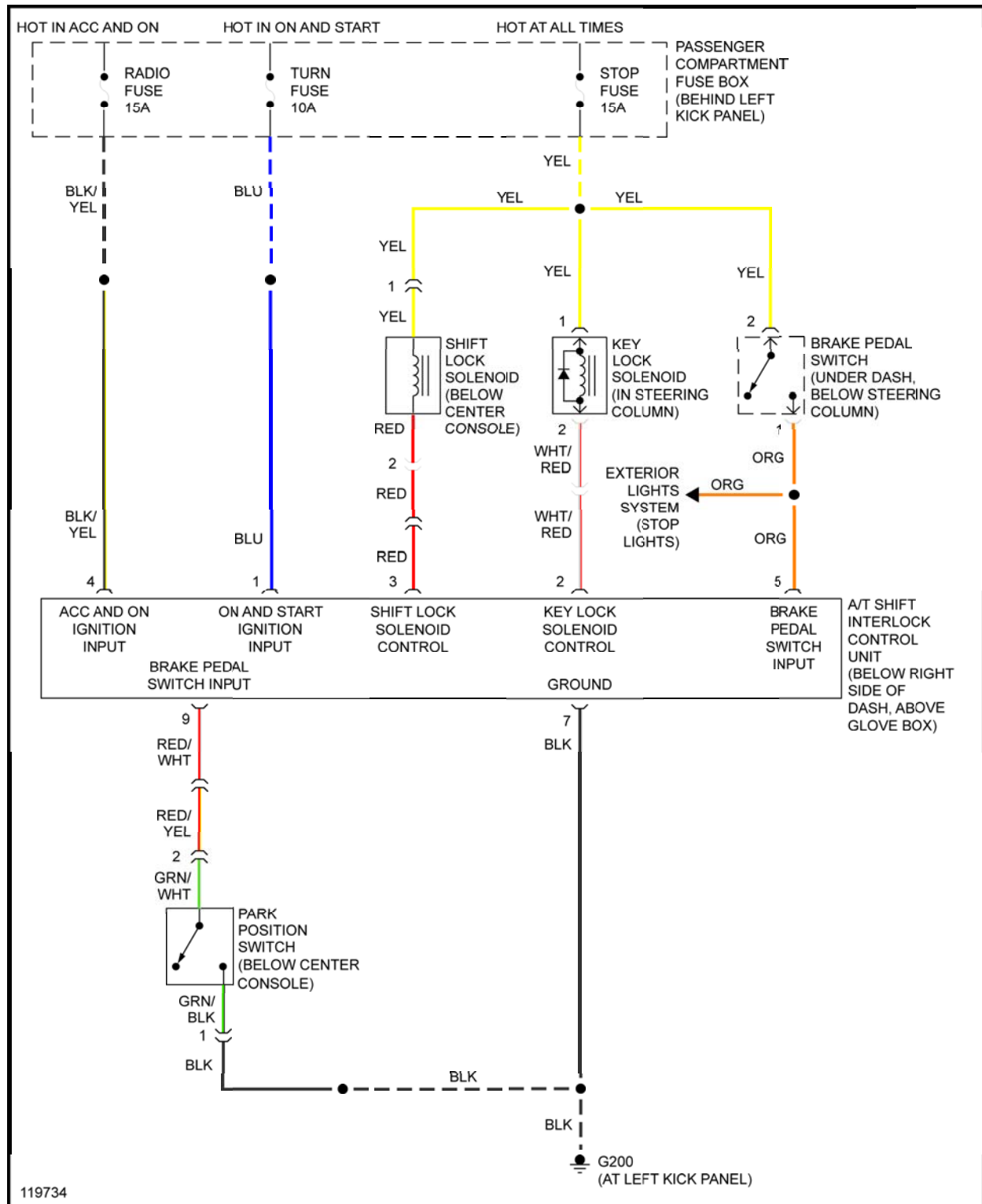


**Fig. 24: Shift Interlock Circuit**

**STARTING/CHARGING**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

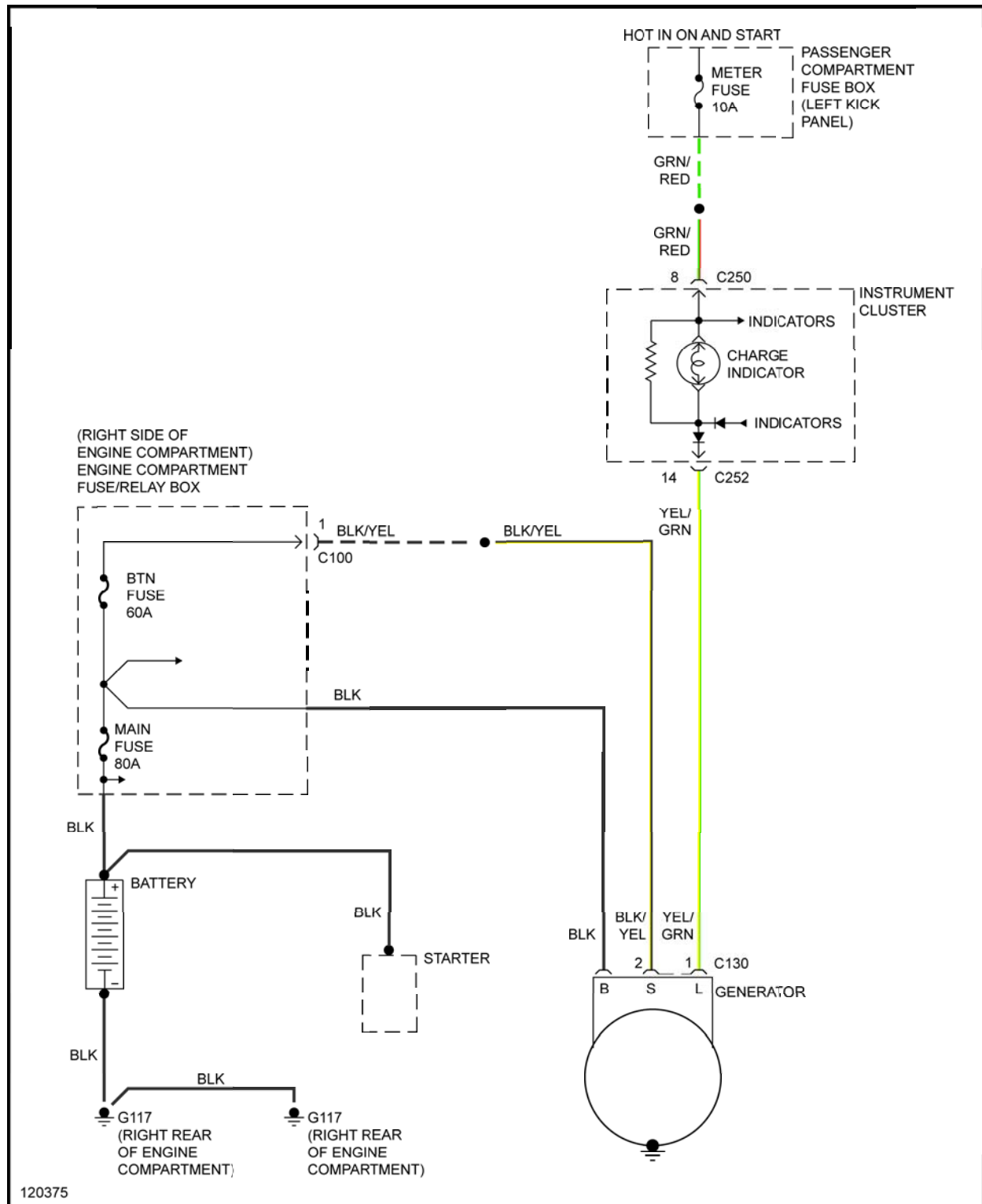

**Fig. 25: Charging Circuit**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS


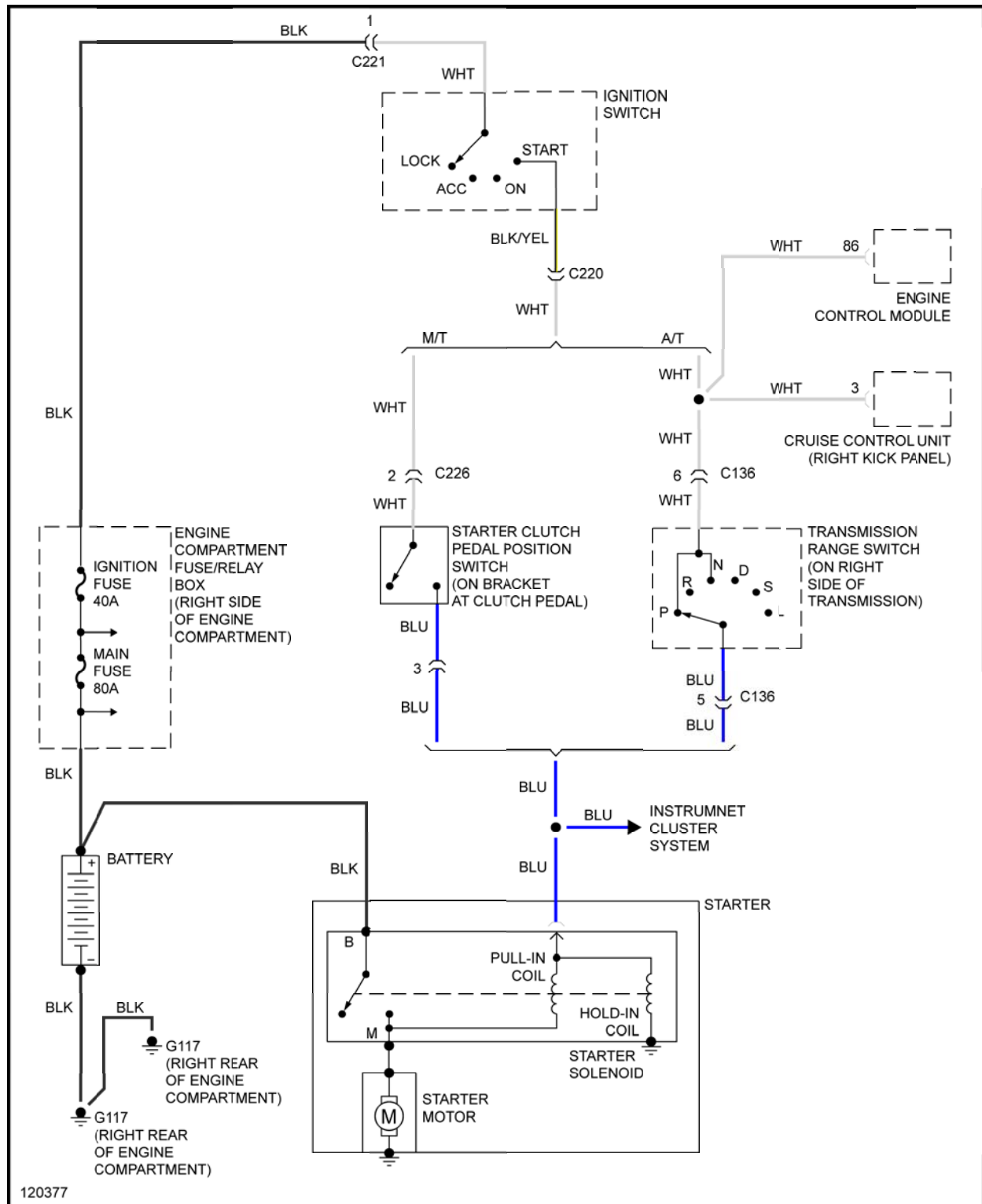


Fig. 26: Starting Circuit

SUPPLEMENTAL RESTRAINTS

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

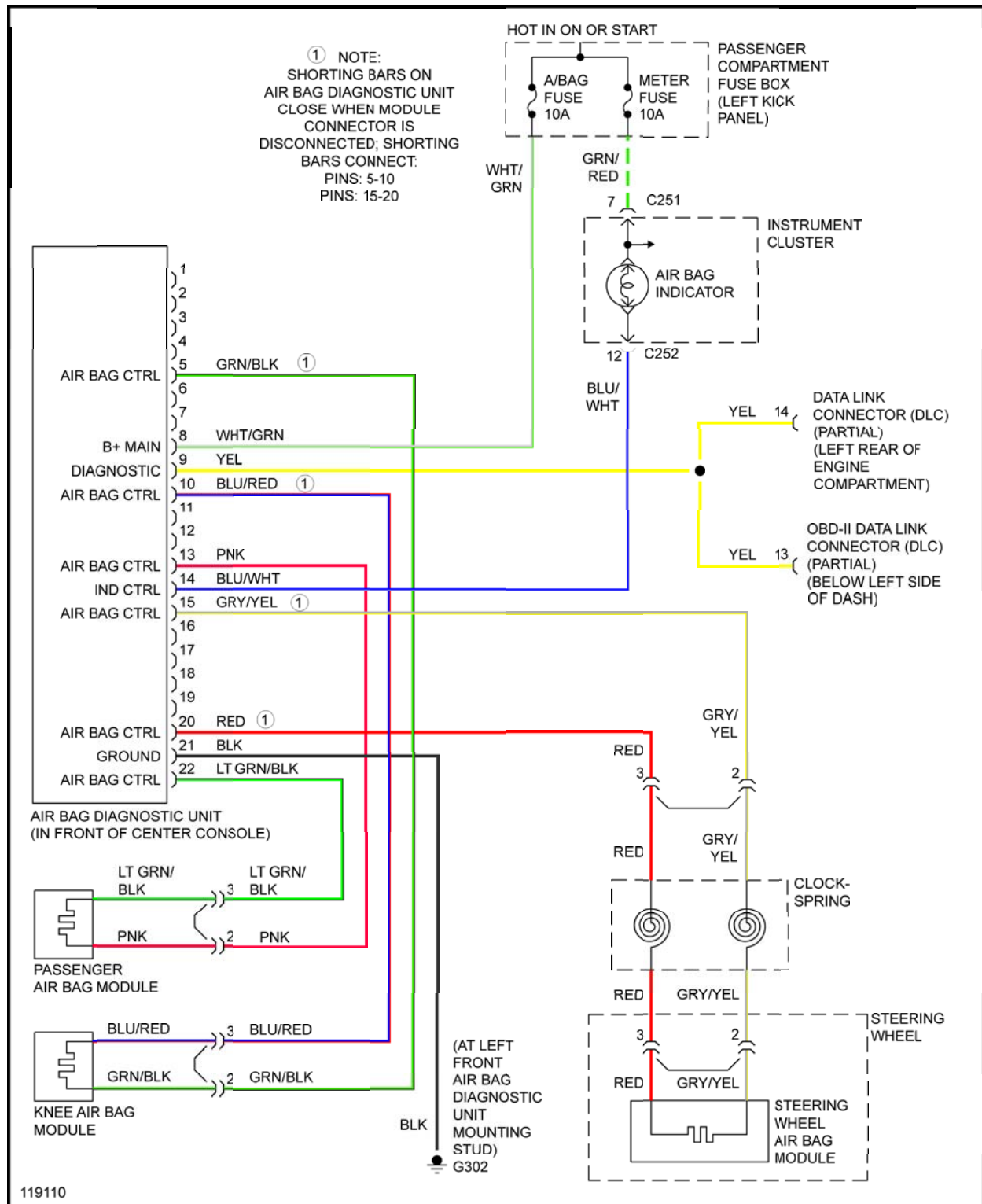

**Fig. 27: Supplemental Restraint Circuit**

**TRANSMISSION**

## SYSTEM WIRING DIAGRAMS

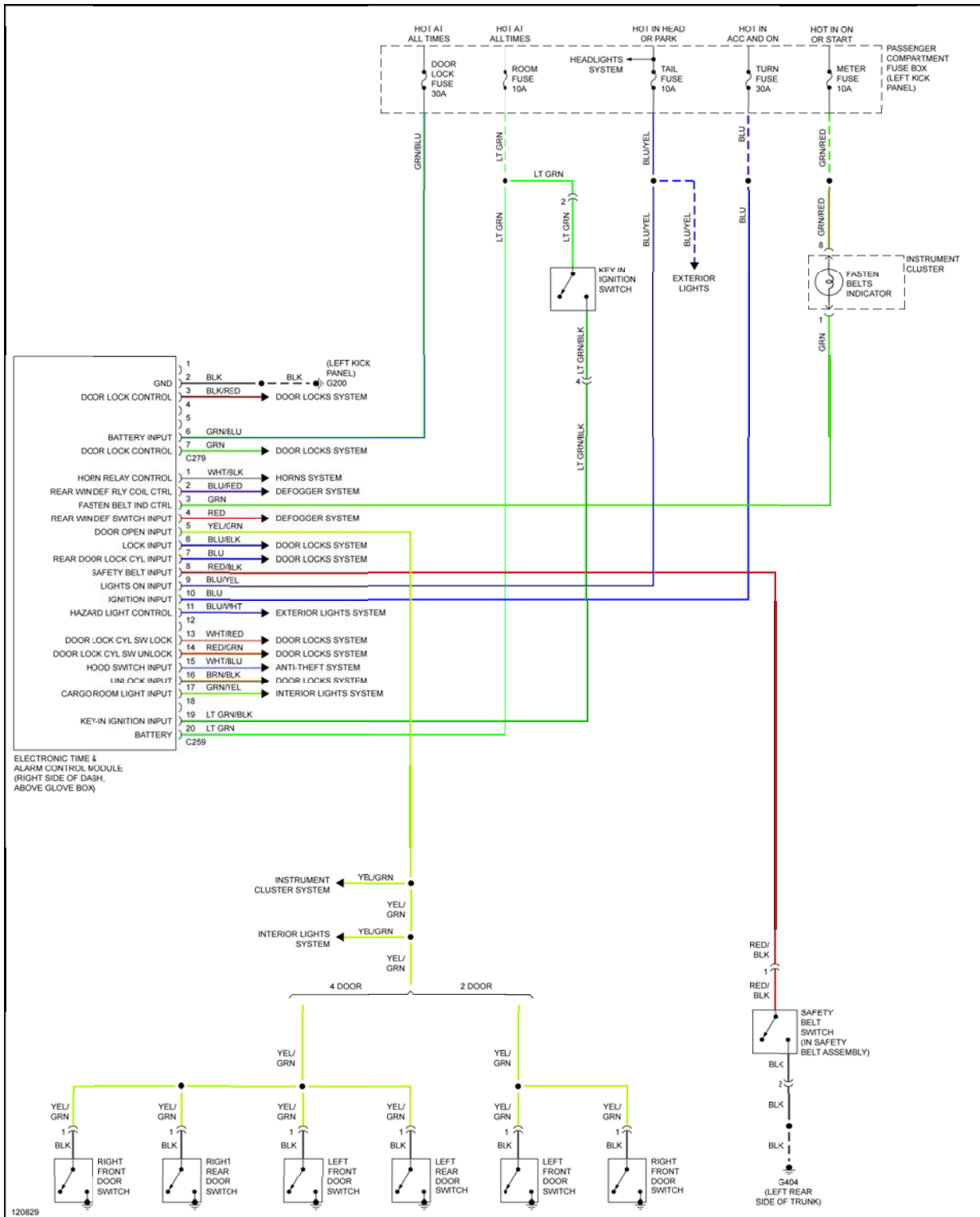


**Fig. 28: A/T Circuit**

**WARNING SYSTEMS**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS



**Fig. 29: Warning System Circuits**

**WIPER/WASHER**


## SYSTEM WIRING DIAGRAMS



**Fig. 30: Front Washer/Wiper Circuit**

# 1998 Kia Sportage

## SYSTEM WIRING DIAGRAMS

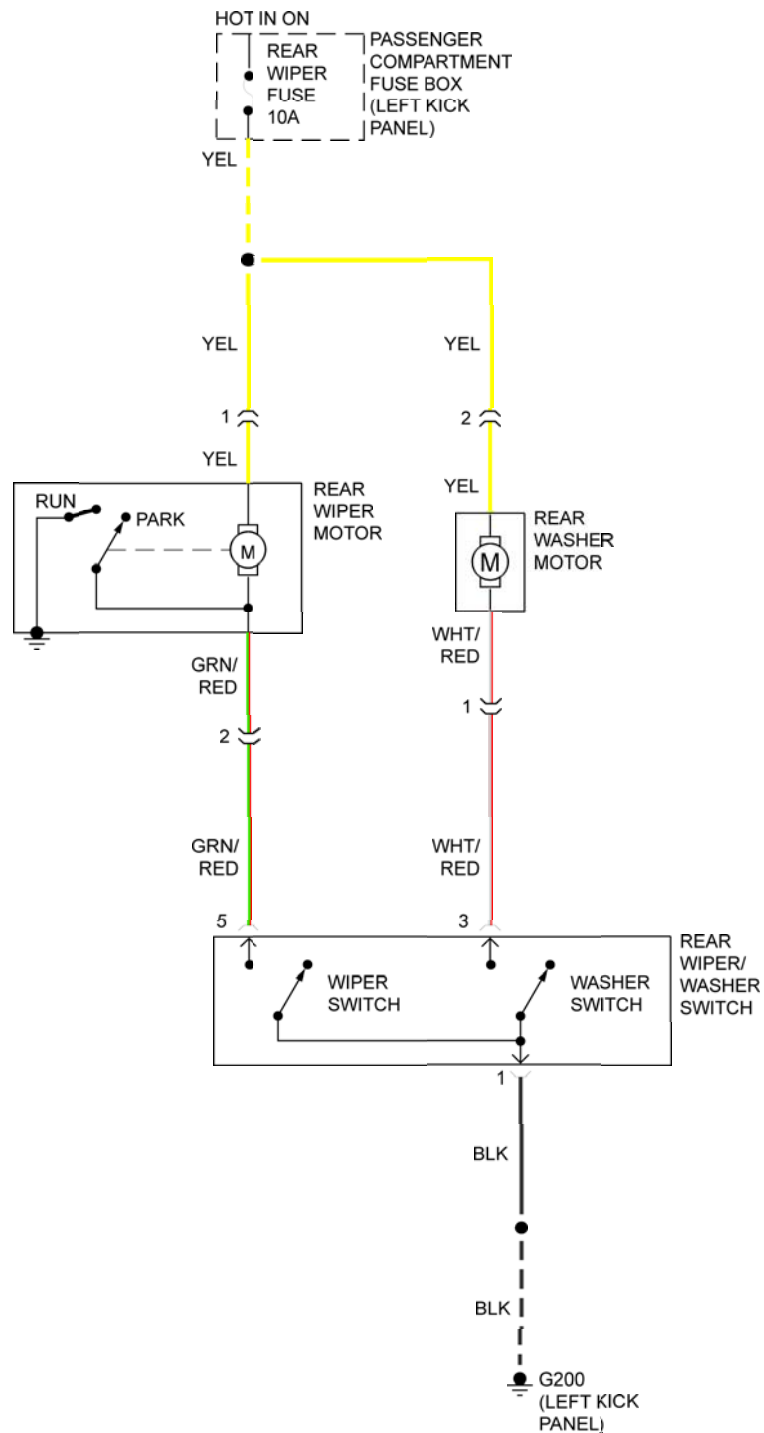

120835

**Fig. 31: Rear Washer/Wiper Circuit**